 


Today's Agenda

- Recap
- Context
 - Binary Adder-Subtractor
 - Decimal Adder
 - Binary Multiplier
- Reading: Textbook, Chapter 4.5-4.7

Recap





Outline

- **Binary Adder**
- Binary Subtractor
- Decimal Adder (BCD)
- Binary Multiplier
- Other Arithmetic Functions

Binary Add

- Similar to the addition operation of decimal numbers.
- $0+0 = 0$, $0+1 = 1$, $1+0 = 1$, $1+1 = 10$ ← The higher significant bit is called a **carry** (进位).
- A combinational circuit that performs the addition of two bits as described above is called a **half-adder**.
- The addition operation involves three bits — the **augend bit**, **addend bit**, and the **carry bit** and produces a sum result as well as carry.
- The combinational circuit performing this type of addition operation is called a **full-adder**.

11	carry(进位)
1011	augend(被加数)
0001	addend(加数)
<hr/>	
1100	sum

Recall: Design Procedure

1. Specification: From the specifications, determine the inputs, outputs, and their symbols.
2. Formulation: Derive the truth table (functions) from the relationship between the inputs and outputs
3. Optimization: Derive the simplified Boolean functions for each output function. Draw a logic diagram for the resulting circuits using AND, OR, and inverters.
4. Technology Mapping: Transform the logic diagram to a new diagram using the available implementation technology.
 - Verification: Verify the design.

DIGITAL LOGIC

Chapter 4 part3: Arithmetic Circuit

2023 Fall

Half-adder

- 1. Spec

- Inputs: x, y
- Outputs: $C(\text{carry}), S(\text{sum})$

- 2. Truth table



		2^1	2^0
x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- 3. Boolean function


$$S = x'y + xy' = x \oplus y$$

$$C = xy$$

- 4. Block diagram

  

Full-adder

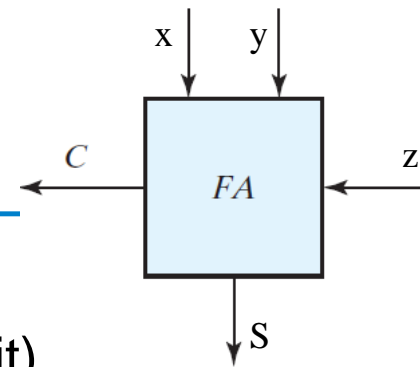

- 1. Spec
 - Inputs: x , y , z (carry from previous lower significant bit)
 - Outputs: C (carry), S (sum)


2. Truth table

3. Boolean function


$$S = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

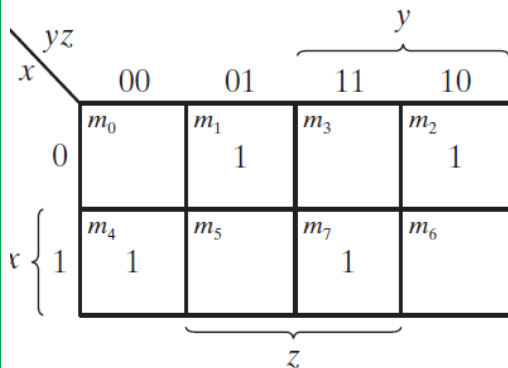

(a) $S = x'y'z + x'yz' + xy'z' + xyz$

 

(b) $C = xy + xz + yz$

xor gate, odd number
of 1 \rightarrow sum = 1

if \geq two inputs are 1
 \rightarrow carry = 1



Full-adder

- 3. Boolean function

$$S = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

- 4. Block diagram

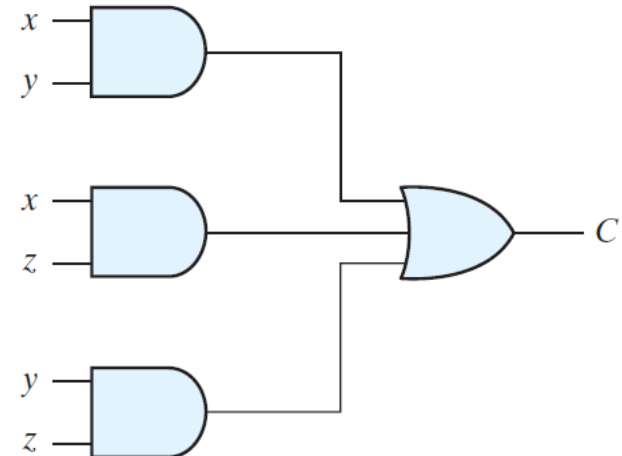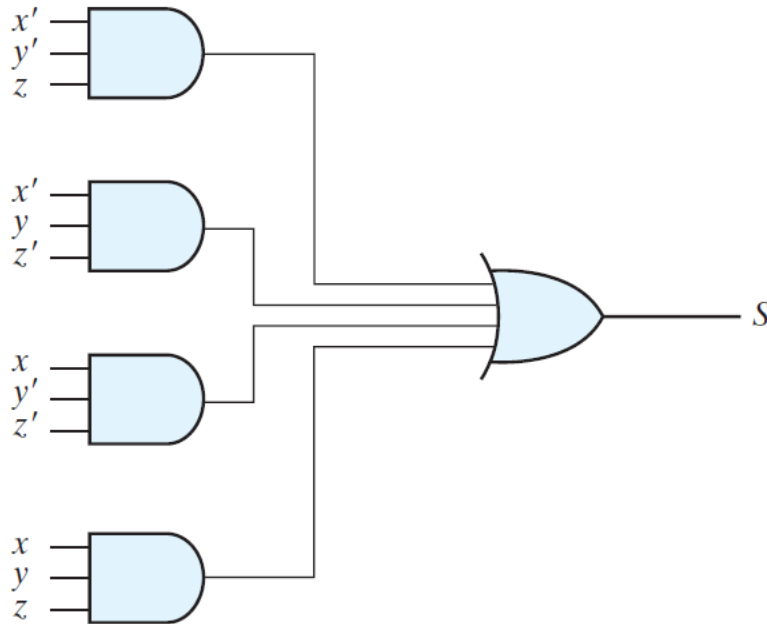



Full Adder Implemented with Half Adders

- Full adder implemented with: Two half adders and one OR gate

$$\begin{aligned} S &= xy'z' + x'yz' + xyz + x'y'z \\ &= z'(xy' + x'y) + z(xy + x'y') \\ &= z'(xy' + x'y) + z(xy' + x'y)' \\ &= z \oplus (x \oplus y) \end{aligned}$$

$$C = z(xy' + x'y) + xy = z(x \oplus y) + xy$$
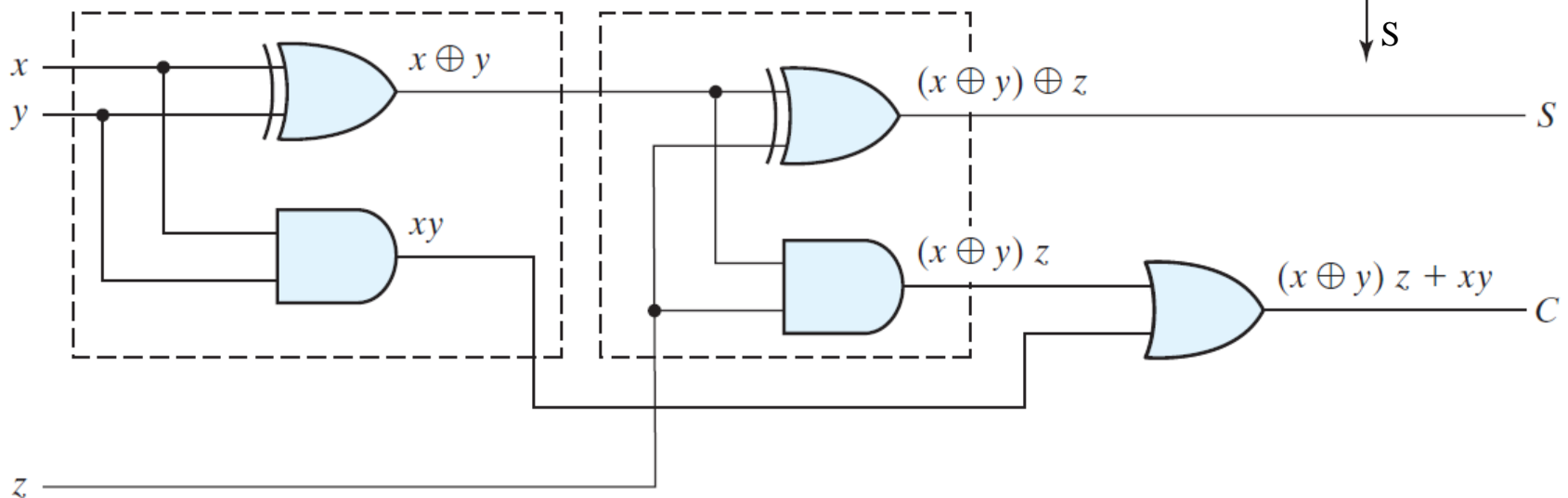 
$$\begin{aligned} S &= x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z \\ C &= xy + xz + yz \end{aligned}$$



Ripple-Carry Adder




- unsigned addition
- $(C_n S_{n-1} S_{n-2} \dots S_0) = (A_{n-1} A_{n-2} \dots A_0) + (B_{n-1} B_{n-2} \dots B_0)$
- eg. $S = A + B$, $A = A_3 A_2 A_1 A_0$, $B = B_3 B_2 B_1 B_0$, $S = S_3 S_2 S_1 S_0$

			C_{i+1}	C_i	
C	1	0	1	0	
A		1	0	1	A_i
B		1	0	0	B_i
S	1	0	1	0	

The computation time of a ripple-carry adder grows linearly with word length n

$T = O(n)$ due to **carry chain**

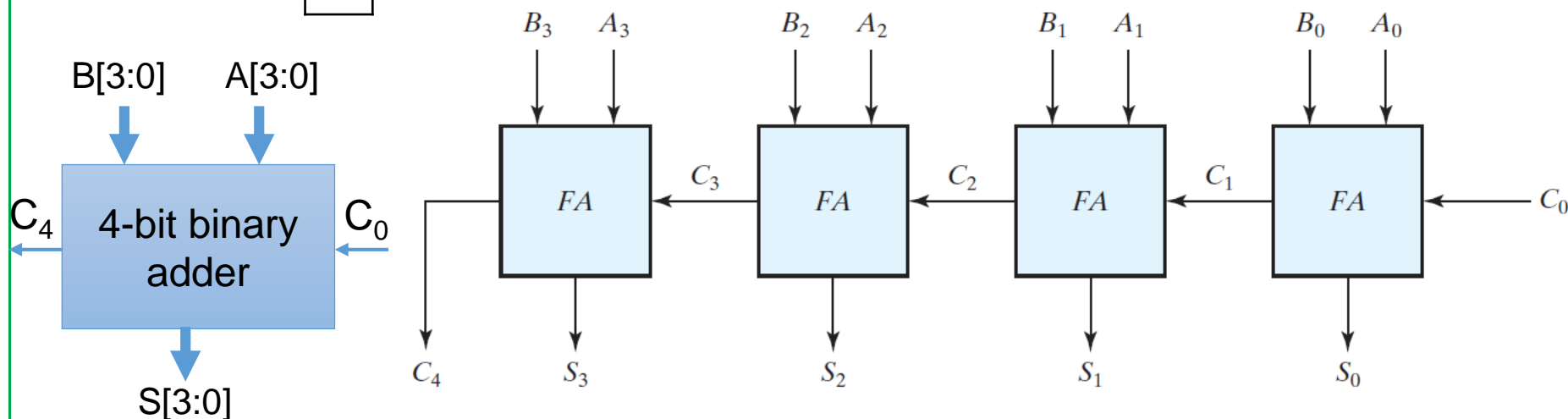

Ripple-Carry Adder


Ai \ BiCi	00	01	11	10
	m_0	m_1	m_3	m_2
0		1		1
1	m_4 1	m_5	m_7 1	m_6

$$S_i = A_i \oplus B_i \oplus C_i$$

Ai \ BiCi	00	01	11	10
	m_0	m_1	m_3	m_2
0			1	
1		1	1	1

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

Ai	Bi	Ci	Ci+1	Si
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

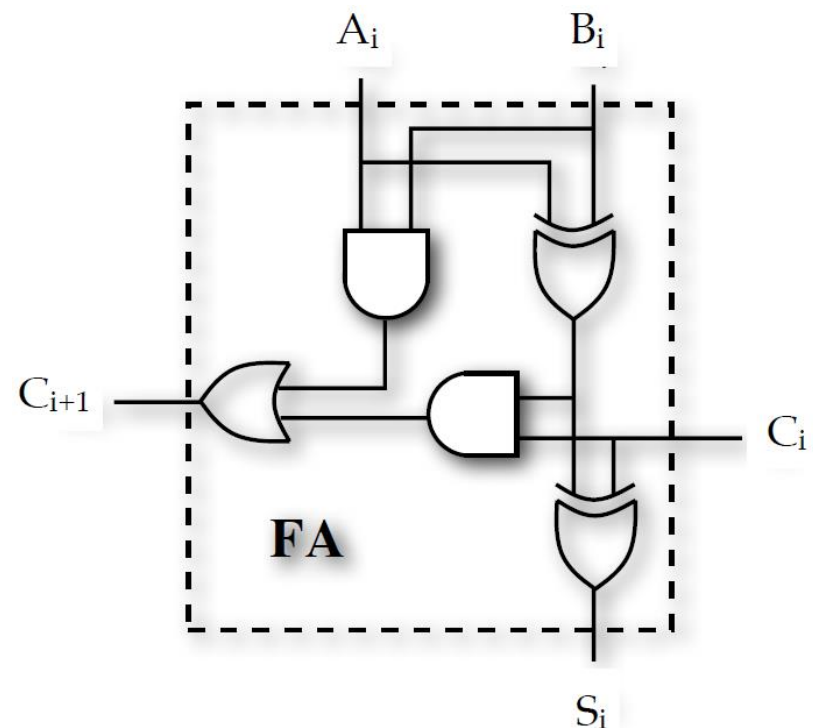

Carry Lookahead Adder

- For a full adder, define what happens to carry

- Carry-generate: $C_{out}=1$ independent of C_{in}

- $G_i = A_i \cdot B_i$

- Carry-propagate: $C_{out}=C_{in}$


- $P_i = A_i \oplus B_i$ or $P_i = A_i + B_i$

A_i	B_i	G_i	P_i
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	x

- Use the above G_i and P_i

- $C_{i+1} = A_i B_i + B_i C_i + A_i C_i = A_i B_i + (A_i + B_i) C_i = G_i + P_i C_i$

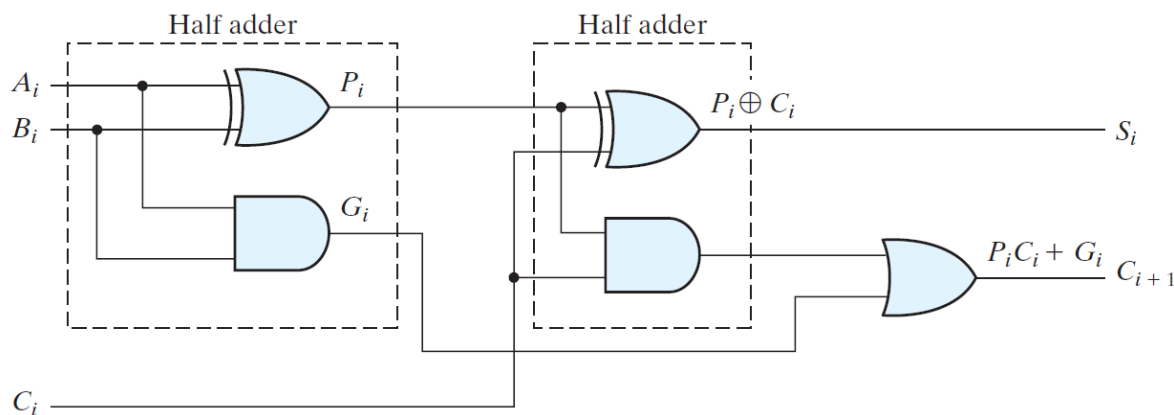- $S_i = A_i \oplus B_i \oplus C_i = P_i \oplus C_i$



Carry Lookahead Adder

- Do not have to wait for C_i to compute C_{i+1}
 - $C_{i+1} = G_i + P_i C_i$
 - $C_{i+2} = G_{i+1} + P_{i+1} C_{i+1} = G_{i+1} + P_{i+1} G_i + P_{i+1} P_i C_i$
 - $C_{i+3} = G_{i+2} + P_{i+2} C_{i+2} = G_{i+2} + P_{i+2} G_{i+1} + P_{i+2} P_{i+1} G_i + P_{i+2} P_{i+1} P_i C_i$
 - $C_{i+4} = G_{i+3} + P_{i+3} C_{i+3} = G_{i+3} + P_{i+3} G_{i+2} + P_{i+3} P_{i+2} G_{i+1} + P_{i+3} P_{i+2} P_{i+1} G_i + P_{i+3} P_{i+2} P_{i+1} P_i C_i$
- Fixed delay time for each carry (but not the same for every gate!)
- Fanout of G_i & P_i also affect the overall delay → usually be limited to 4 bits

C_0 = input carry,

$C_1 = G_0 + P_0 C_0$,

$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$,

$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$

Carry Lookahead Adder

C_0 = input carry,



$C_1 = G_0 + P_0 C_0$,

$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$,

$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$

$$G_i = A_i \cdot B_i$$
 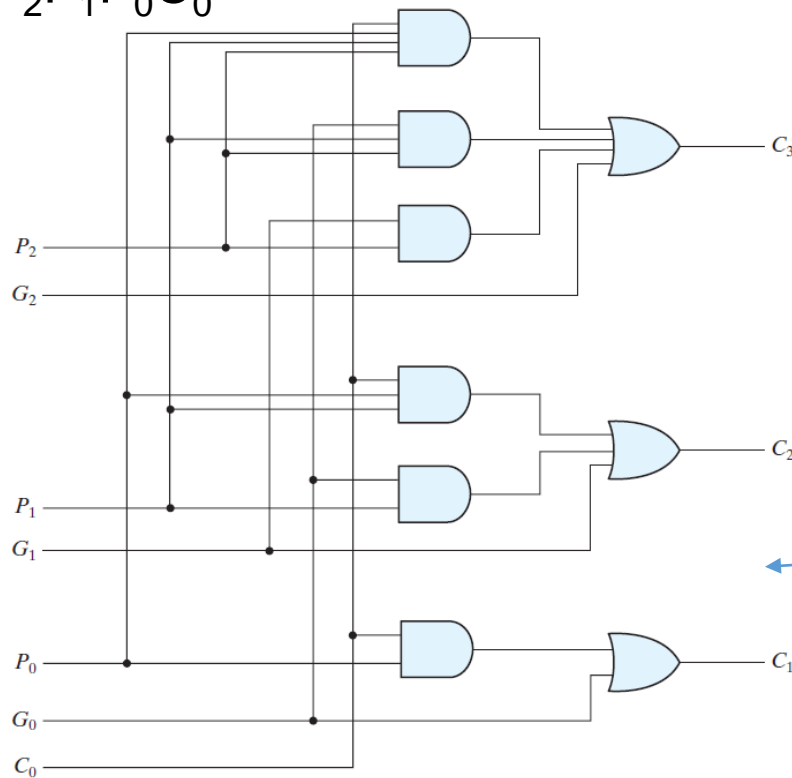
$$P_i = A_i \oplus B_i \text{ or } P_i = A_i + B_i$$






Outline

- Binary Adder
- **Binary Subtractor**
- Decimal Adder (BCD)
- Binary Multiplier
- Other Arithmetic Functions

Binary Adders/Subtractors

- Binary subtraction normally is performed by adding the minuend to the 2's complement of the subtrahend.

M	Function	Comments
0	$S=A+B$	addition
1	$S=A+B'+1$	subtraction

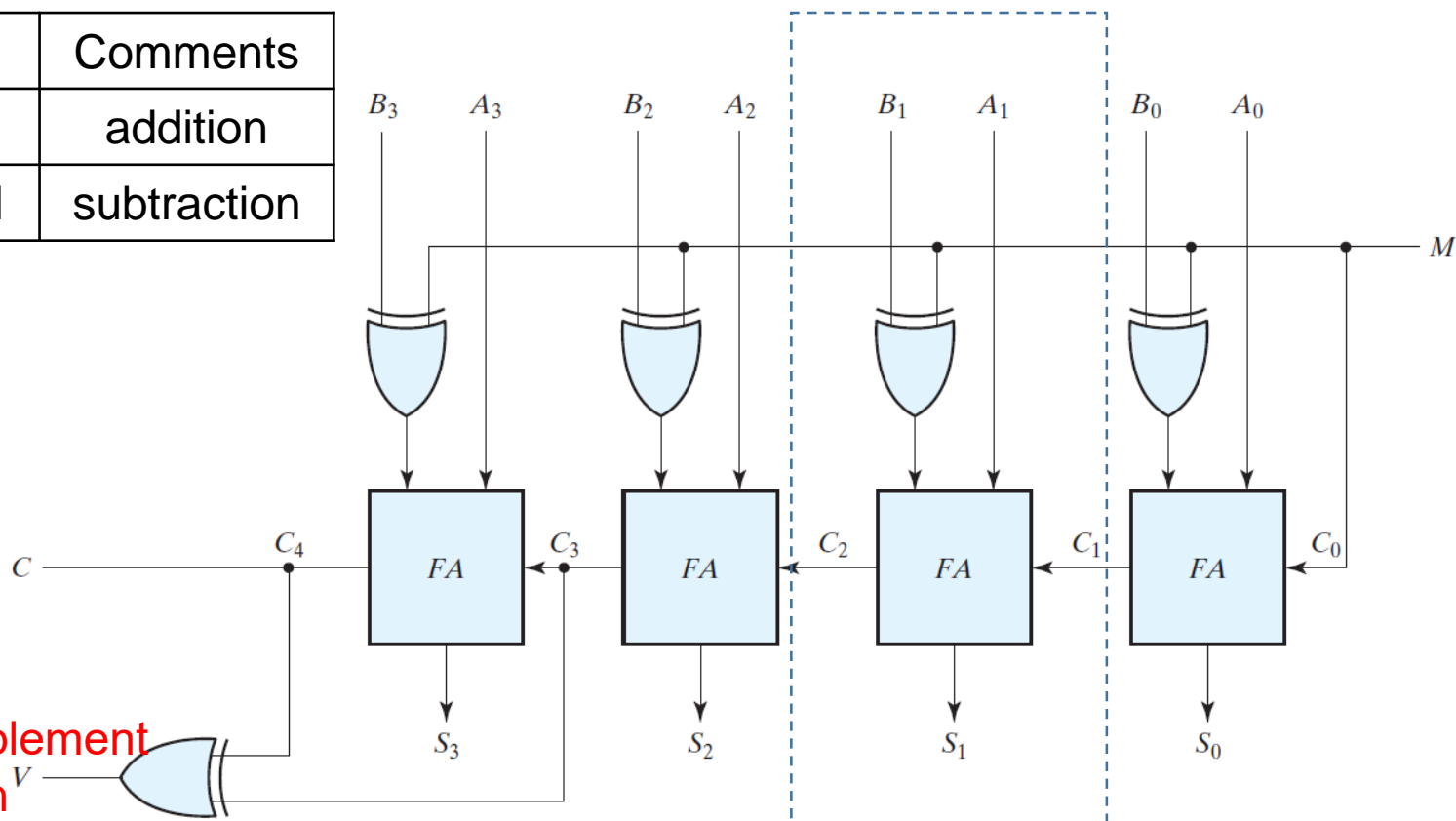

Overflow

- When n-digits addition with sum occupying n+1 digits, we say that an overflow (溢出) occurred.

- Carry** for unsigned numbers:

- Carry indicates unsigned number overflow

$$\begin{array}{r}
 \text{1 1 1} \\
 1\ 0\ 1\ 1\ \dots\ 11 \\
 +\ 0\ 1\ 1\ 1\ \dots\ 7 \\
 \hline
 1\ 0\ 0\ 1\ 0\ \dots\ 18\ \text{(needs 5bits)}
 \end{array}$$

- Overflow** for Signed numbers: (2's Complement)

- two -ve numbers are added and the obtained result is +ve
- two +ve numbers are added and the obtained result is -ve

$$\begin{array}{r}
 \text{1 0 0 1} \\
 1\ 0\ 0\ 1\ \dots\ -7 \\
 +\ 1\ 1\ 0\ 1\ \dots\ -3 \\
 \hline
 1\ 0\ 1\ 1\ 0\ \dots\ -10 \\
 \underbrace{\hspace{1.5cm}}_6
 \end{array}$$


4 bits can not correctly represent -10

$$\begin{array}{r}
 \text{0 1 1 1} \\
 0\ 1\ 1\ 1\ \dots\ 7 \\
 +\ 0\ 0\ 0\ 1\ \dots\ 1 \\
 \hline
 1\ 0\ 0\ 0\ \dots\ 8 \\
 \underbrace{\hspace{1.5cm}}_{-8}
 \end{array}$$

4 bits can not correctly represent +8

Binary Adders/Subtractors

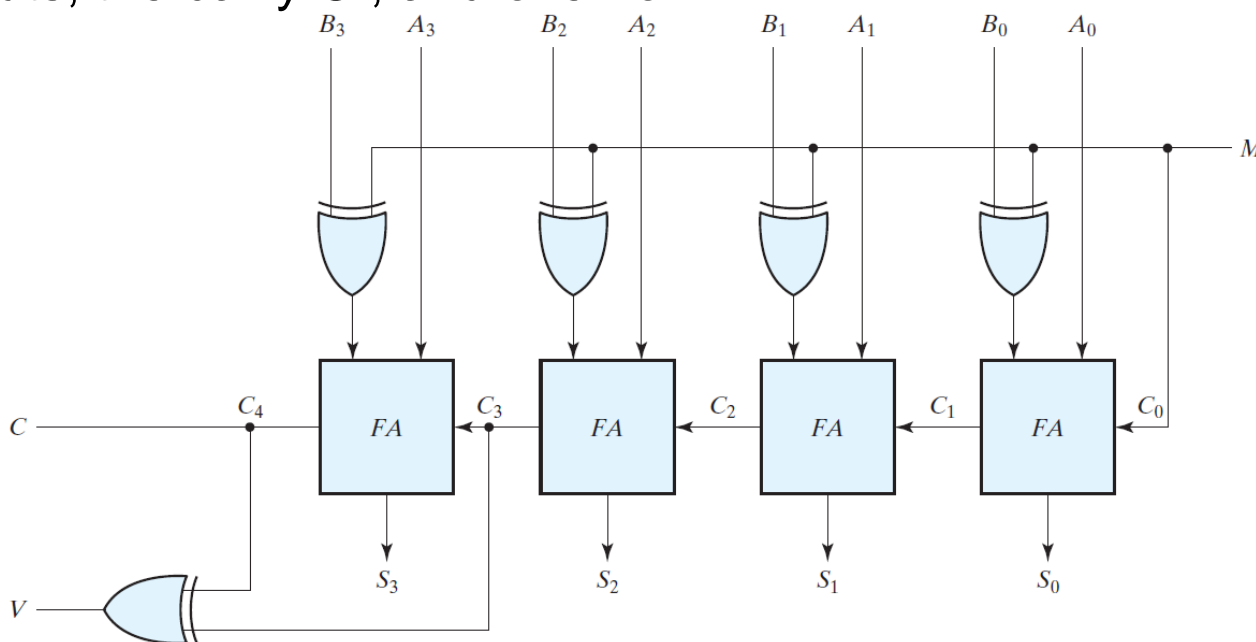
- Overflow happens when A and B are 2's complement signed value
- Example: In each case, determine the values of the four SUM outputs, the carry C, and overflow V



M	A	B	SUM	C	V
0	0111	0110	1101	0	1
1	1100	1000	0100	1	0

Serial Adder

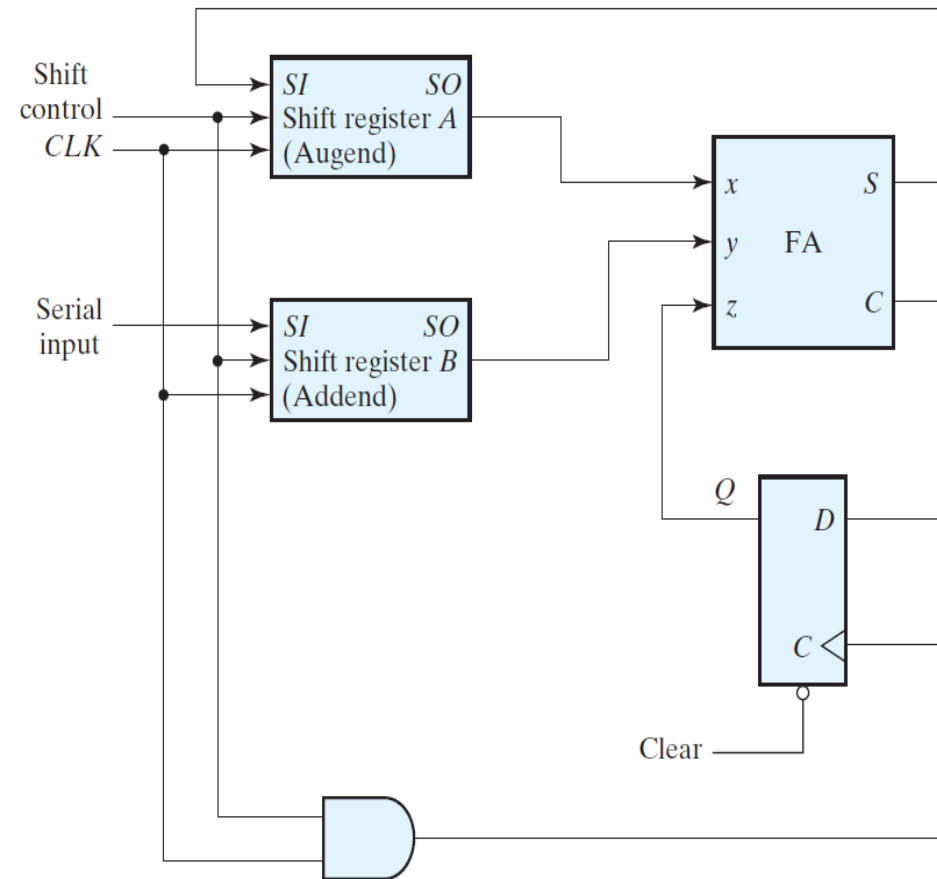
- Initially, augend is in register A and addend is in register B
- Shift control enables/disables the clock for FF
- addition of two operands from LSB to MSB
- A new sum (S) bit is transferred to shift register A
- A carry-out (C) of the FA is transferred to Q as the z input of the next addition
- Finally, when the shift control is disabled, summation result is stored in shift register A



Timing Sequence of Serial Adder

- Serial addition of 0101 + 0111
 - Register A(Store Augend and Sum): 0101
 - Register B(Store Addend): 0111
 - More cycles required to initialize Register A and B
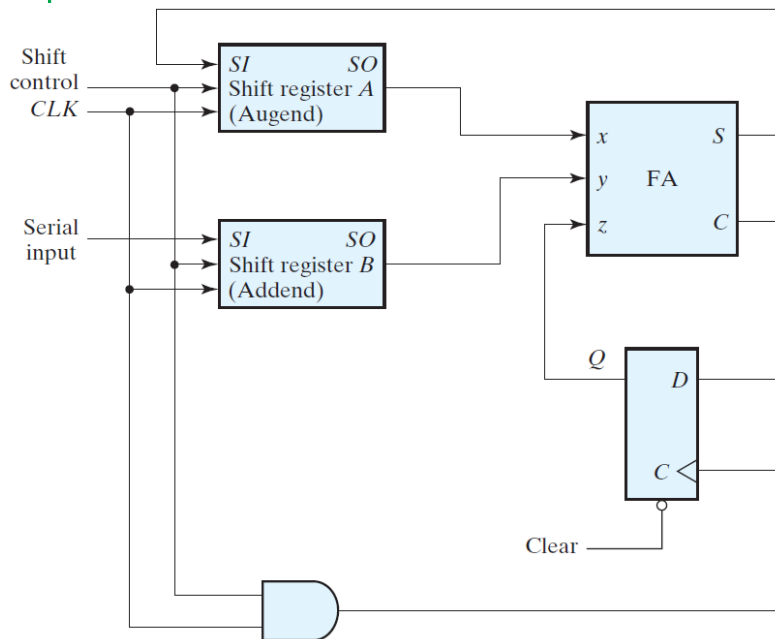
$$\begin{array}{r}
 1110 \\
 0101 \\
 + 0111 \\
 \hline
 1100
 \end{array}$$



T	Register A	Register B	C	S
0	0101	0111	0	0
1	0010	0011	1	0
2	0001	0001	1	1
3	1000	0000	1	1
4	1100	0000	0	0

sum



Outline

- Binary Adder
- Binary Subtractor
- **Decimal Adder (BCD)**
- Binary Multiplier
- Other Arithmetic Functions

Decimal Adders

- Addition of 2 decimal digits in BCD
- $\{C_{out}, S\} = A + B + C_{in}$
- $S = S_8 S_4 S_2 S_1$, $A = A_8 A_4 A_2 A_1$, $B = B_8 B_4 B_2 B_1$
- A digit in BCD cannot exceed 9, add 6 (0110) for final correction.

Decimal Symbol	BCD Digit
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

10		1 0 0 0 0	
8_{10}	A	1 0 0 0 ₂	
9_{10}	B	1 0 0 1 ₂	
<hr/>		<hr/>	
	KZ	1 0 0 0 1 ₂	binary coded results
		0 1 1 0 ₂	if > 9, add 6
17 ₁₀	CS	0 0 0 1 0 1 1 1 ₂	BCD coded result

K: binary carry, Z: binary sum, C: BCD carry, S: BCD sum

Decimal Adders

K	Binary Sum				C	BCD Sum				Decimal
	Z ₈	Z ₄	Z ₂	Z ₁		S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

$Z_8 Z_4 + Z_8 Z_2$


K

- C = 1 when
 1. K=1
 2. or K = 0, but $A+B > 9$, which is $Z_8 Z_4 + Z_8 Z_2$
- C = 1 means need to add 0110

Z ₂ Z ₁ / Z ₈ Z ₄	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	0	0	1	1

Decimal Adders

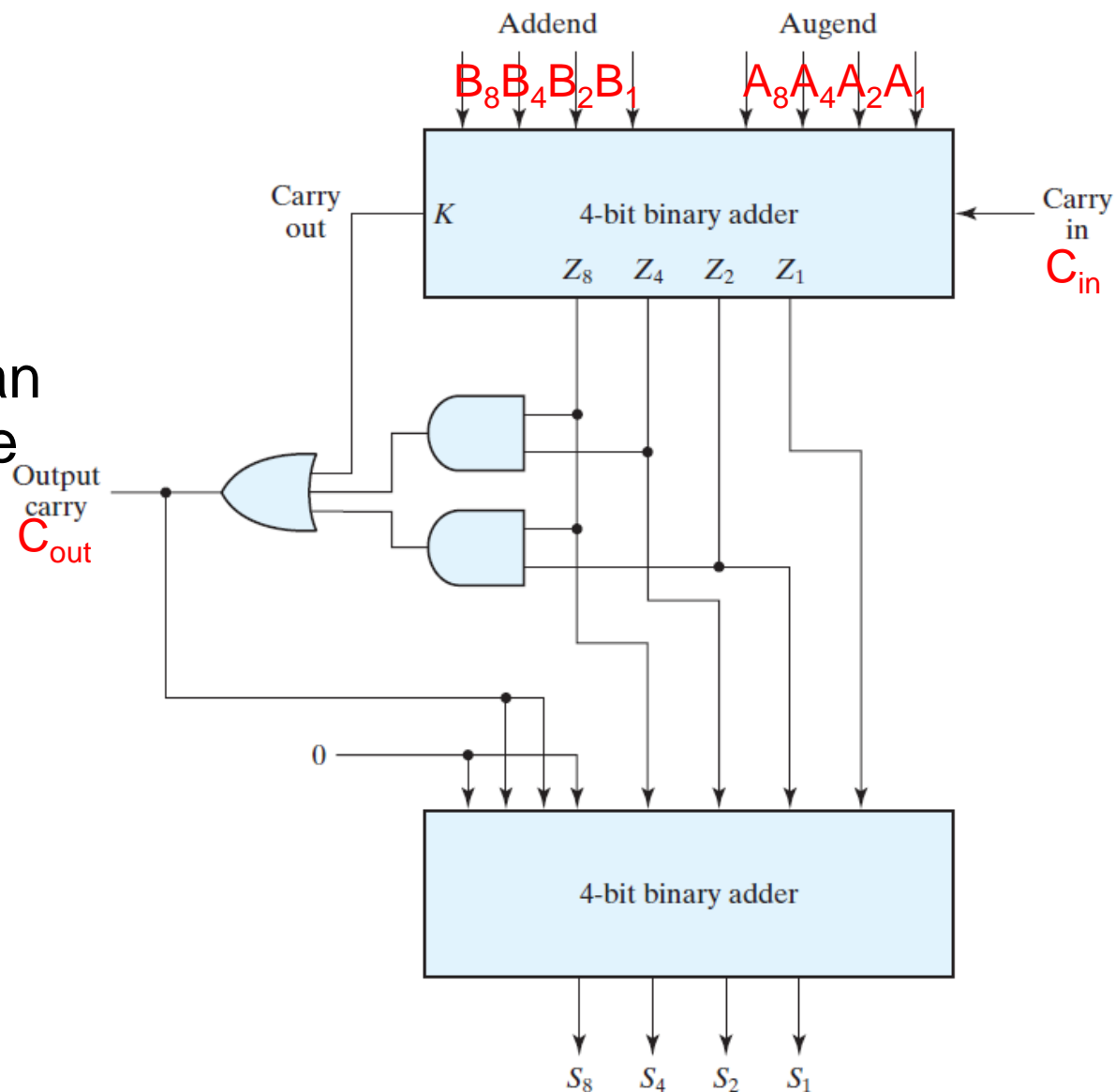- $C_{out} = K + Z_8 Z_4 + Z_8 Z_2$
- When $C = 1$, it is necessary to add 0110 to the binary sum and provide an output carry for the next stage.






Outline

- Binary Adder
- Binary Subtractor
- Decimal Adder (BCD)
- **Binary Multiplier**
- Other Arithmetic Functions

2-bit x 2-bit Binary Multiplier

4-bit x 3-bit Binary Multiplier

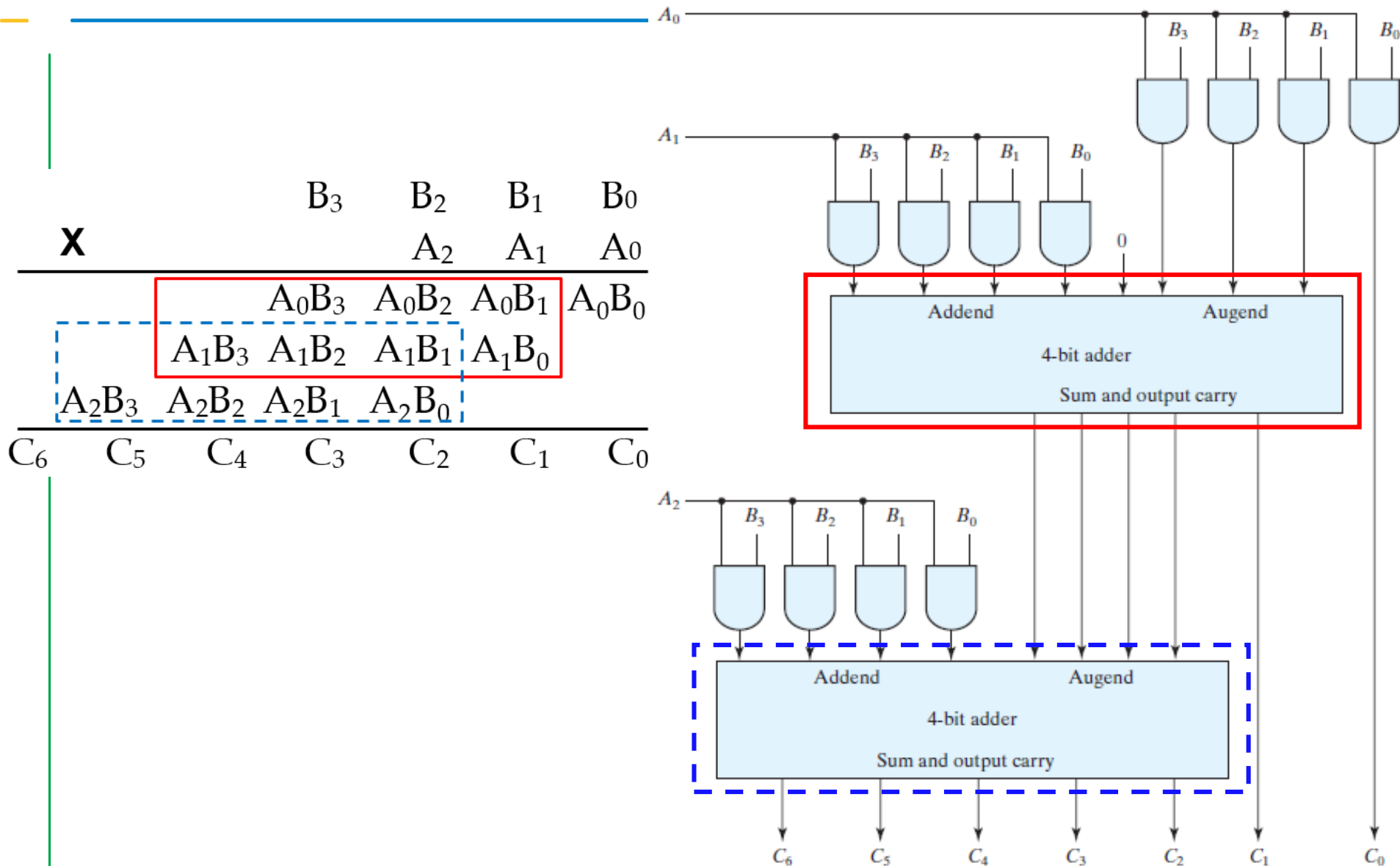



Outline

- Binary Adder
- Binary Subtractor
- Decimal Adder (BCD)
- Binary Multiplier
- **Other Arithmetic Functions (optional)**

Other Arithmetic Functions


- It is convenient to design the functional blocks by **contraction**
 - Removal of redundancy from circuit to which input fixing has been applied
- Functions
 - Increment
 - Decrement
 - Multiplication by constant
 - Division by constant
 - Zero fill and extension

Design by Contraction


- Simplify the logic in a functional block to implement a different function
 - The new function must be realizable from the original function by applying basic functions to its inputs
 - Contraction is treated here only for application of 0s and 1s (not for X and X')
 - After application of 0s and 1s, equations or the logic diagram are simplified

Design by Contraction Example

 - Contraction of a ripple carry adder to incrementer for $n=1$ ($A_2A_1A_0+001$)



(a)

 


Incrementing and Decrementing


- Incrementing
 - Add a fixed value to an arithmetic variable
 - Fixed value is often 1, called counting up
 - $A+1$, $B+4$
 - Functional block is called incrementer
- Decrementing
 - Subtracting a fixed value from an arithmetic variable
 - Fixed value is often 1, called counting down
 - $A-1$, $B-4$
 - Functional block is called decrementer

Multiplication/Division by 2^n

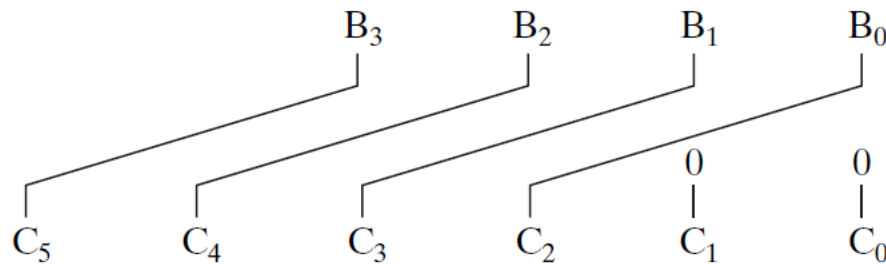- Shift left (multiplication) or right (division)




shift left by 2

 

shift right by 2

Multiplication by a Constant

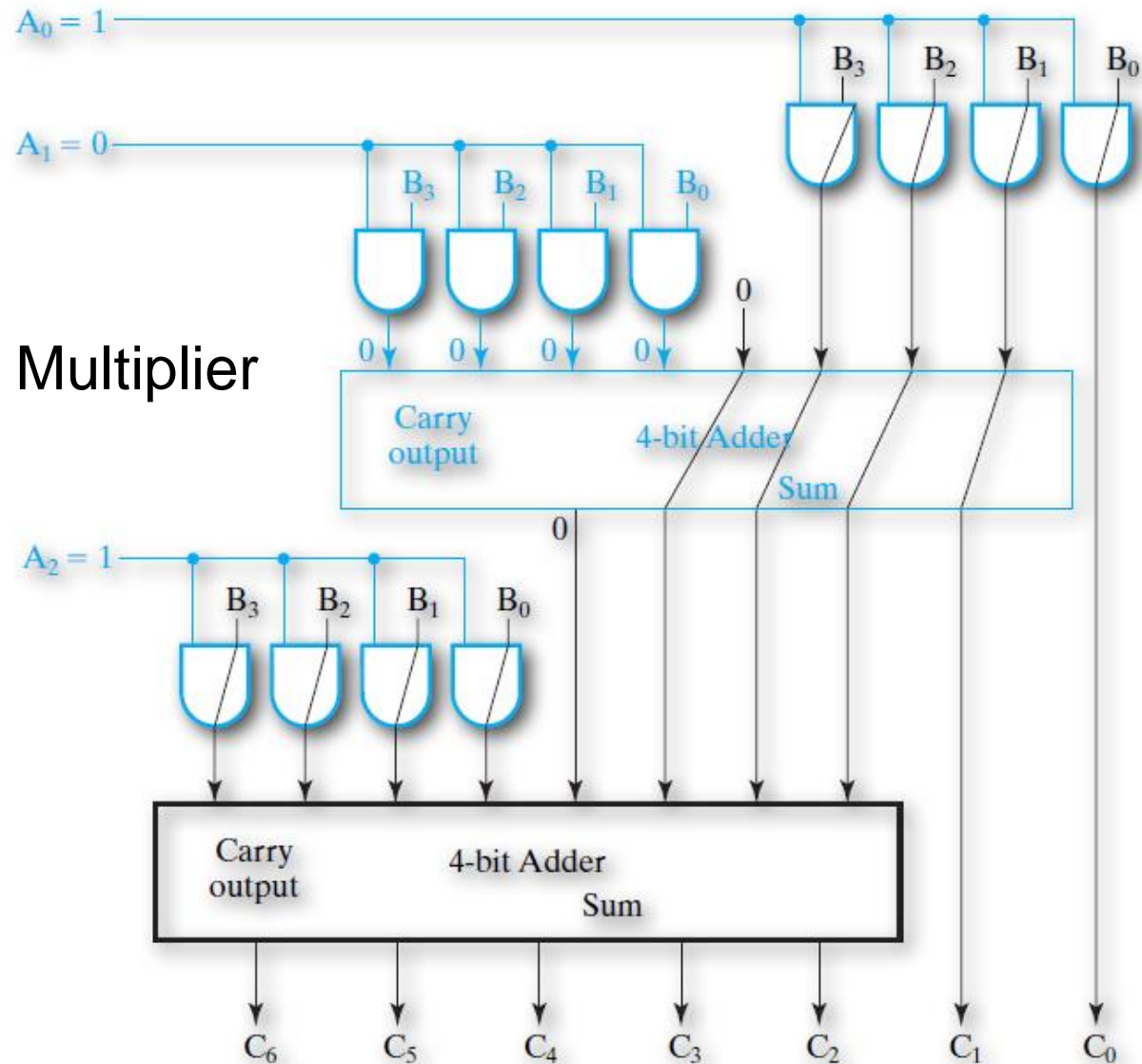- 4-bit x 3-bit Binary Multiplier
- $B_3B_2B_1B_0 \times 101$



Zero/Sign Extension

- Fill an m-bit operand with 0s to become an n-bit operand with $n > m$
 - Filling usually is applied to the MSB end of the operand
- Zero Extension
 - 01110101 filled to 16 bits
 - 0000000001110101 $\{\{8\{0\}\}\}$ 01110101}
 - 11110101 filled to 16 bits
 - 0000000011110101 $\{\{8\{0\}\}\}$ 11110101}
- Sign Extension
 - Copies the MSB of the operand into the new positions
 - 01110101 extended to 16 bits
 - 0000000001110101 $\{\{8\{a7\}\}\}$ a71110101}
 - 11110101 extended to 16 bits
 - 1111111111110101 $\{\{8\{a7\}\}\}$ a71110101}