

# Assignment#3 CS207 Fall 2023

Ben Chen(12212231)

December 8, 2023

PROBLEM 1. Analyze the sequential circuit with two JK flip-flops A and B with two inputs x and y and one output z. The input equation and output equation is given.

SOLUTION. The state equation for the circuit is given by

$$\begin{aligned}A(t+1) &= J_A(t)A' + K'_A(t)A = A'Bx + A'B'y' + A(B'xy')' \\&= A'Bx + A'B'y' + A(B + x' + y) \\&= A'Bx + A'B'y' + AB + Ax' + Ay \\&= \Sigma(0, 2, 6, 7, 8, 9, 10, 12, 13, 14, 15)\end{aligned}$$

$$\begin{aligned}B(t+1) &= J_B(t)B' + K'_B(t)B = A'B'x + B(A + xy')' \\&= A'B'x + A'Bx'y \\&= \Sigma(2, 3, 4, 5, 7)\end{aligned}$$

and the output equation is given by



$$z(t) = Ax'y' + Bx'y' = \Sigma(4, 8, 12)$$

So the state table is

Table 1: State Table

Present State		Input		Next State		Output	JKFF Input			
$A$	$B$	$x$	$y$	$A$	$B$	$z$	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	1	0	0	1	0	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	1	0	1	1	1	1
0	0	1	1	0	1	0	0	0	1	0
0	1	0	0	0	1	1	0	0	0	0
0	1	0	1	0	1	0	0	0	0	0
0	1	1	0	1	0	0	1	0	1	1
0	1	1	1	1	1	0	1	0	1	0
1	0	0	0	1	0	1	1	0	0	1
1	0	0	1	1	0	0	0	0	0	1
1	0	1	0	1	0	0	1	1	0	1
1	0	1	1	0	0	0	0	0	0	1
1	1	0	0	1	0	1	0	0	0	1
1	1	0	1	1	0	0	0	0	0	1
1	1	1	0	1	0	0	1	0	0	1
1	1	1	1	1	0	0	1	0	0	1

and the state diagram and timing diagram is

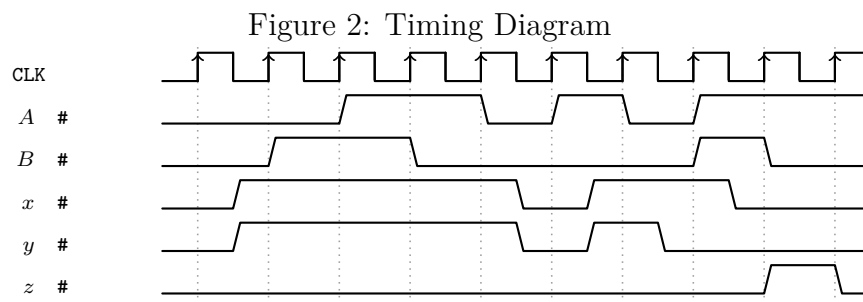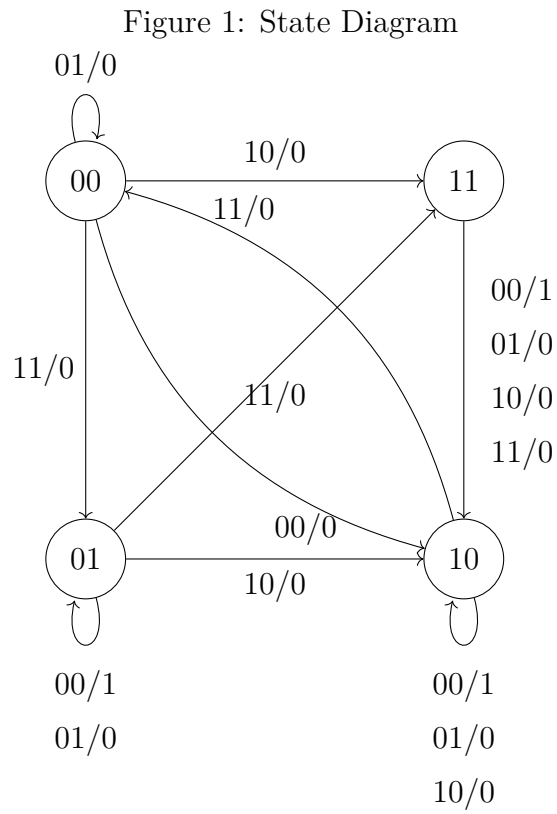

PROBLEM 2. Analyze the sequential circuit with two TFFs A and B.

SOLUTION. From the diagram, we can derive the input equations

$$T_A = A + B$$

$$T_B = A' + B$$

and there's no output equation. So the state equation would be


$$A(t+1) = T_A \oplus Q_A = (A + B) \oplus A$$

$$B(t+1) = T_B \oplus Q_B = (A' + B) \oplus B$$

and the state table is


Table 2: State Table			
Present State		Next	
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>
0	0	0	1
0	1	1	0
1	0	0	0
1	1	0	0

the fourth state is useless. And the timing diagram and state diagram is

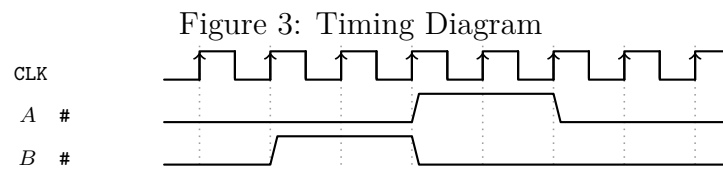

PROBLEM 3. For the block diagram, find the state table and state diagram.

Figure 4: State Diagram

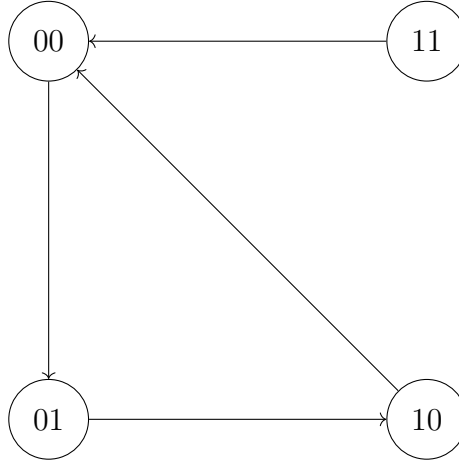

SOLUTION. a) The input functions are

$$J_1 = X$$

$$K_1 = (Q'_2 X)'$$

$$J_2 = X$$

$$K_2 = (Q_1 X)'$$

and the state equation is

$$Q_1(t+1) = J_1 Q'_1 + K'_1 Q_1 = Q'_1 X + Q_1 Q'_2 X$$

$$Q_2(t+1) = J_2 Q'_2 + K'_2 Q_2 = Q'_2 X + Q_1 Q_2 X$$

$$\begin{aligned} Q'_2(t+1) &= (X' + Q_2)(Q'_1 + Q'_2 + X') \\ &= X' + Q_2(Q'_1 + Q'_2) = X' + Q'_1 Q_2 \end{aligned}$$

and the output function is

$$F = X \oplus Q_2(t+1)' = X \oplus (X' + Q'_1 Q_2)$$


so the state table is


b) It's a Mealy Machine since the output  $F$  is determined by the input  $X$  and the state.

Table 3: State Table

Present State		Input	Next State		Output	JKFF Input			
$Q_1(t)$	$Q_2(t)$		$Q_1(t+1)$	$Q_2(t+1)$		$J_1$	$K_1$	$J_2$	$K_2$
0	0	0	0	0	1	0	1	0	1
0	0	1	1	1	1	1	0	1	1
0	1	0	1	0	1	0	1	0	1
0	1	1	0	0	0	1	1	1	1
1	0	0	0	0	1	0	1	0	1
1	0	1	1	1	1	1	0	1	0
1	1	0	0	0	1	0	1	0	1
1	1	1	0	1	1	1	1	1	0

Figure 5: State Diagram

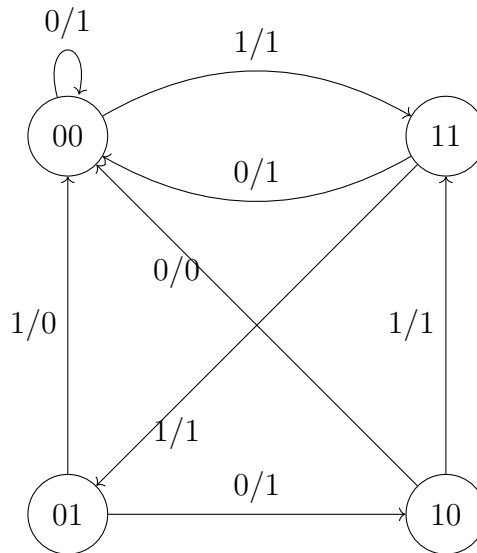

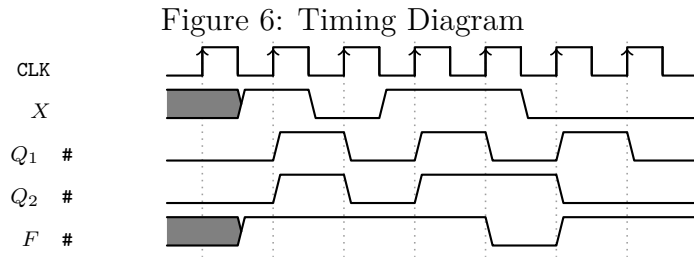

c) The timing diagram based on the state table is

PROBLEM 4. Obtain the simplified input equations for a sequential circuit with TFF and the state diagram is given.

SOLUTION. From the state diagram, we can derive the state table so the

Table 4: State Table

Present State		Input	Next State	
$Q_1(t)$	$Q_2(t)$		$Q_1(t+1)$	$Q_2(t+1)$
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

state equations are

$$Q_1(t+1) = T_1 \oplus Q_1(t) = \Sigma(2, 3, 4, 5, 7)$$

$$Q_2(t+1) = T_2 \oplus Q_2(t) = \Sigma(0, 2, 4, 7)$$

and the K-Maps for each TFF are

		$Q_2 \backslash Q_1$			
		00	01	11	10
$Q_1$	0	0	0	1	1
	1	1	1	1	0

		$Q_2 \backslash Q_1$			
		00	01	11	10
$Q_1$	0	1	0	0	1
	1	1	0	1	0

So the simplified state equations are

$$\begin{aligned}
 Q_1(t+1) &= Q_1'Q_2 + Q_2X + Q_1Q_2' \\
 &= Q_1 \oplus (Q_1 \oplus (Q_1'Q_2 + Q_2X + Q_1Q_2')) \\
 &= Q_1 \oplus (Q_1'Q_2 + Q_1Q_2X')
 \end{aligned}$$

$$\begin{aligned}
 Q_2(t+1) &= Q_2'X' + Q_1'X' + Q_1Q_2X \\
 &= Q_2 \oplus (Q_2 \oplus (Q_2'X' + Q_1'X' + Q_1Q_2X)) \\
 &= Q_2 \oplus (Q_1Q_2X' + Q_1'Q_2X)
 \end{aligned}$$

So the input equations are

$$\begin{aligned}
 T_1 &= Q_1'Q_2 + Q_1Q_2X' \\
 T_2 &= Q_1Q_2X' + Q_1'Q_2X
 \end{aligned}$$

PROBLEM 5. Design a DFF with enable input whose function table is given.




SOLUTION. From the characteristic table, we can derive the input equation

$DQ \backslash En$	00	01	11	10
0	0	1	1	0
1	0	0	1	1

$$Q(t) = Q(t+1)En' + DEn$$

so the circuit is

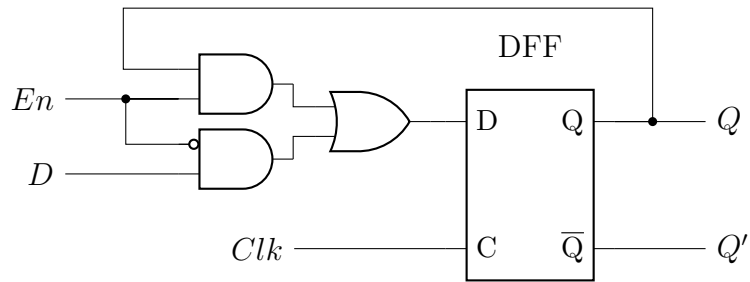

PROBLEM 6. Design a certain flip-flop according to the following description.

SOLUTION. a) The characteristic table is

$A$	$B$	$Q(t+1)$	$Q(t+1)'$	
0	0	0	1	clear to 0
0	1	$Q(t)$	$Q'(t)$	no change
1	0	$Q'(t)$	$Q(t)$	complement
1	1	1	0	set to 1

b) From the characteristic table, we can derive the K-maps first

$Q(t) \backslash AB$	00	01	11	10
0	0	0	1	1
1	0	1	1	0

so the simplified equation is

$$Q(t+1) = AQ'(t) + BQ(t)$$

c) The excitation table is

$Q(t)$	$Q(t+1)$	$A$	$B$	Operation
0	0	0	X	no change
0	1	1	X	set to 1
1	0	X	0	clear to 1
1	1	X	1	no change

d) From the characteristic equation, we have

$$Q(t+1) = AQ'(t) + (B')'Q(t)$$

that is, we can substitute the inputs with JKFF's inputs


$$Q(t+1) = JQ'(t) + K'Q(t) \Rightarrow J = A \quad K = B'$$

which indicates the input equations of our flip-flop

$$A = J$$

$$B = K'$$

so the block diagram is

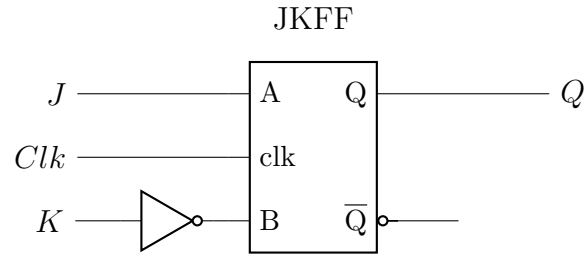


**PROBLEM 7.** For the following state table, simplify the state table and draw the state diagram. Then design the sequential circuit using JKFF.

**SOLUTION.** To simplify the state, we first notice that the state of  $h$  is the same as state  $d$ , so we can remove the state  $h$  and rewrite the transition to  $h$  into  $d$ . Then we assign codes to the states and obtain the state table

Table 5: State Table				
Present State	Next State		Output	
$ABC$	$x = 0$	$x = 1$	$x = 0$	$x = 1$
000	101	001	0	0
001	011	010	0	0
010	101	100	0	0
011	110	000	1	0
100	011	010	0	0
101	101	010	1	1
110	110	011	0	1
111	X	X	X	X

and the corresponding state diagram is

Figure 7: State Diagram

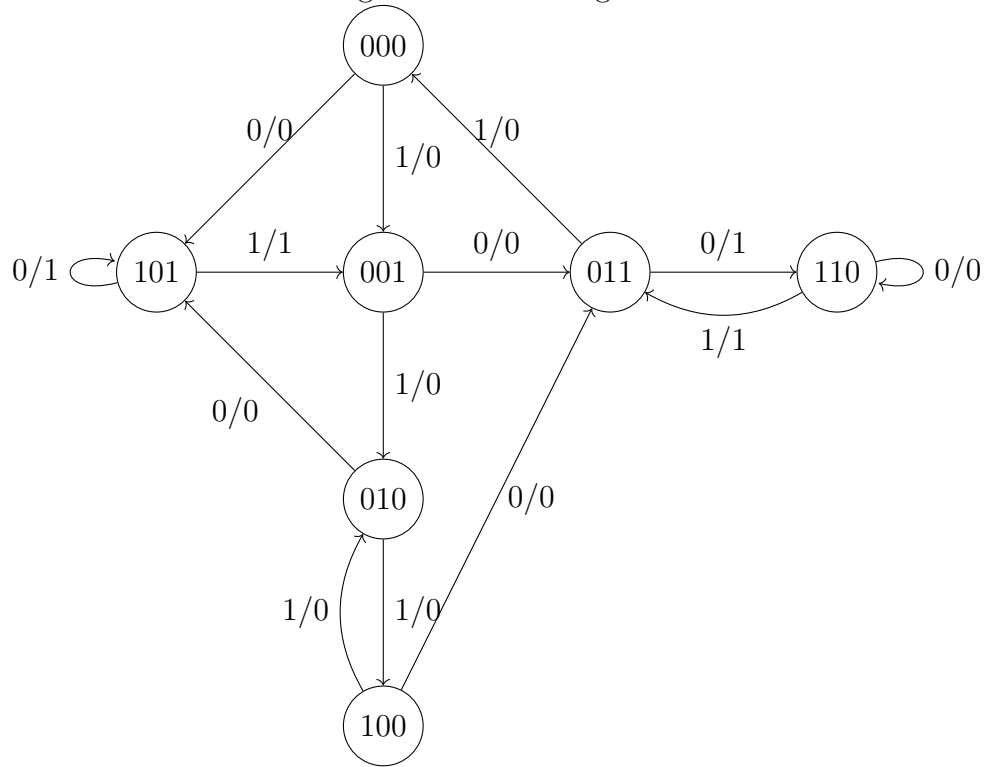

Next we obtain the state equations and output equation using the state table and K-map

$C_2$ AB	00	01	11	10
00	1	0	0	0
01	1	1	0	1
11	X	X	X	X
10	X	X	X	X

$C_2$ AB	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	0	1	X	X
10	1	1	1	0

$\begin{smallmatrix} AB \\ \hline C_2 \end{smallmatrix}$	00	01	11	10
00	0	0	1	1
01	X	X	X	X
11	X	X	X	X
10	1	1	1	0

$\begin{smallmatrix} AB \\ \hline C_2 \end{smallmatrix}$	00	01	11	10
00	X	X	X	X
01	1	1	1	0
11	0	0	X	X
10	X	X	X	X

$\begin{smallmatrix} AB \\ \hline C_2 \end{smallmatrix}$	00	01	11	10
00	1	1	X	X
01	1	0	X	X
11	0	1	X	X
10	1	0	X	X

$\begin{smallmatrix} AB \\ \hline C_2 \end{smallmatrix}$	00	01	11	10
00	X	X	1	0
01	X	X	1	1
11	X	X	X	X
10	X	X	1	0

Figure 8: Output K-Map

$\begin{smallmatrix} AB \\ \hline C_2 \end{smallmatrix}$	00	01	11	10
00	0	0	0	0
01	0	0	0	1
11	0	1	X	X
10	0	0	1	1

Table 6: State Table

Present State			Input	Next State			JKFF Input					
<i>A</i>	<i>B</i>	<i>C</i>		<i>A</i>	<i>B</i>	<i>C</i>	<i>J<sub>A</sub></i>	<i>K<sub>A</sub></i>	<i>J<sub>B</sub></i>	<i>K<sub>B</sub></i>	<i>J<sub>C</sub></i>	<i>K<sub>C</sub></i>
0	0	0	0	1	0	1	1	X	0	X	1	X
0	0	0	1	0	0	1	0	X	0	X	1	X
0	0	1	0	0	1	1	0	X	1	X	X	0
0	0	1	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	0	1	1	X	X	1	1	X
0	1	0	1	1	0	0	1	X	X	1	0	X
0	1	1	0	1	1	0	1	X	X	0	X	1
0	1	1	1	0	0	0	0	X	X	1	X	1
1	0	0	0	0	1	1	X	1	1	X	1	X
1	0	0	1	0	1	0	X	1	1	X	0	X
1	0	1	0	1	0	1	X	0	0	X	X	0
1	0	1	1	0	1	0	X	1	1	X	X	1
1	1	0	0	1	1	0	X	0	X	0	0	X
1	1	0	1	0	1	1	X	1	X	0	1	X
1	1	1	X	X	X	X	X	X	X	X	X	X

so the input equations are

$$J_A = C'x' + BC' + BCx'$$

$$K_A = Ax + AB'C'$$

$$J_B = A'C + AC' + Ax$$

$$K_B = A'C'Cx$$

$$J_C = A'B' + A'C'x' + ABx + AB'x'$$

$$K_C = Cx + BC$$

and the output equation is

$$y = AC + ABx + BCx'$$

and the state equations are


$$\begin{aligned} A(t+1) &= J_A A' + K'_A A \\ &= A'(C'x' + BC' + BCx') + A(Ax + AB'C')' \\ &= A'C'x' + A'BC' + A'BCx' + ABx' + ACx' \end{aligned}$$

$$\begin{aligned} B(t+1) &= J_B B' + K'_B B \\ &= B'(A'C + AC' + Ax) + A(A'C'Cx)' \\ &= A + A'B'C \end{aligned}$$

$$\begin{aligned} C(t+1) &= J_C C' + K'_C C \\ &= C'(A'B' + A'C'x' + ABx + AB'x') + C(Cx + BC)' \\ &= A'B'C' + A'C'x' + ABC'x + AB'C'x' + BCx \end{aligned}$$

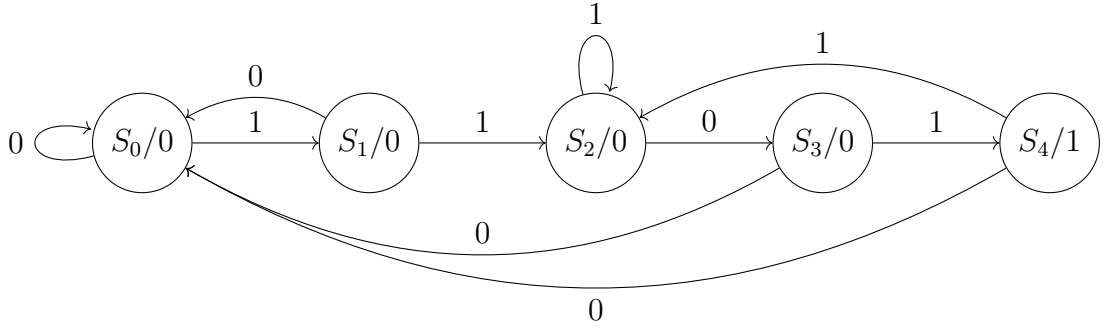**PROBLEM 8.** Design a sequence detector using DFF to recognize the occurrence of bits 1101 with Moore machine in overlapping mode.

**SOLUTION.** According to the description, we can draw the state diagram



and the state table is

Table 7: State Table			
Present State	Next State		Output
$ABC$	$x = 0$	$x = 1$	$y$
$(S_0)$ 000	000	001	0
$(S_1)$ 001	000	010	0
$(S_2)$ 010	011	010	0
$(S_3)$ 011	000	100	0
$(S_4)$ 100	000	010	1
101	X	X	X
110	X	X	X
111	X	X	X

So we can obtain the input and state equations from the K-maps

$$A(t+1) = D_A(t) = BCx$$

$$B(t+1) = D_B(t) = BC' + Ax + B'Cx$$

$$C(t+1) = D_C(t) = BC'x' + A'B'C'x$$



and the output equation is

$$y = A$$

And the K-maps are

$\begin{array}{c} C_x \\ \backslash AB \end{array}$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	0	0	X	X

$\begin{array}{c} C_x \\ \backslash AB \end{array}$	00	01	11	10
00	0	0	1	0
01	1	1	0	0
11	X	X	X	X
10	0	1	X	X

$\begin{array}{c} C_x \\ \backslash AB \end{array}$	00	01	11	10
00	0	1	0	0
01	1	0	0	0
11	X	X	X	X
10	0	0	X	X

$\begin{array}{c} C_x \\ \backslash AB \end{array}$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	X	X	X	X
10	1	1	X	X