

DIGITAL LOGIC


Chapter 3 part2: Two Level Implementation

2023 Fall

Today's Agenda

- Recap
- Context
 - NAND and NOR Implementation
 - Other Two-Level Implementations
 - Exclusive-OR Function
- Reading: Textbook, Chapter 3.6-3.9

Recap

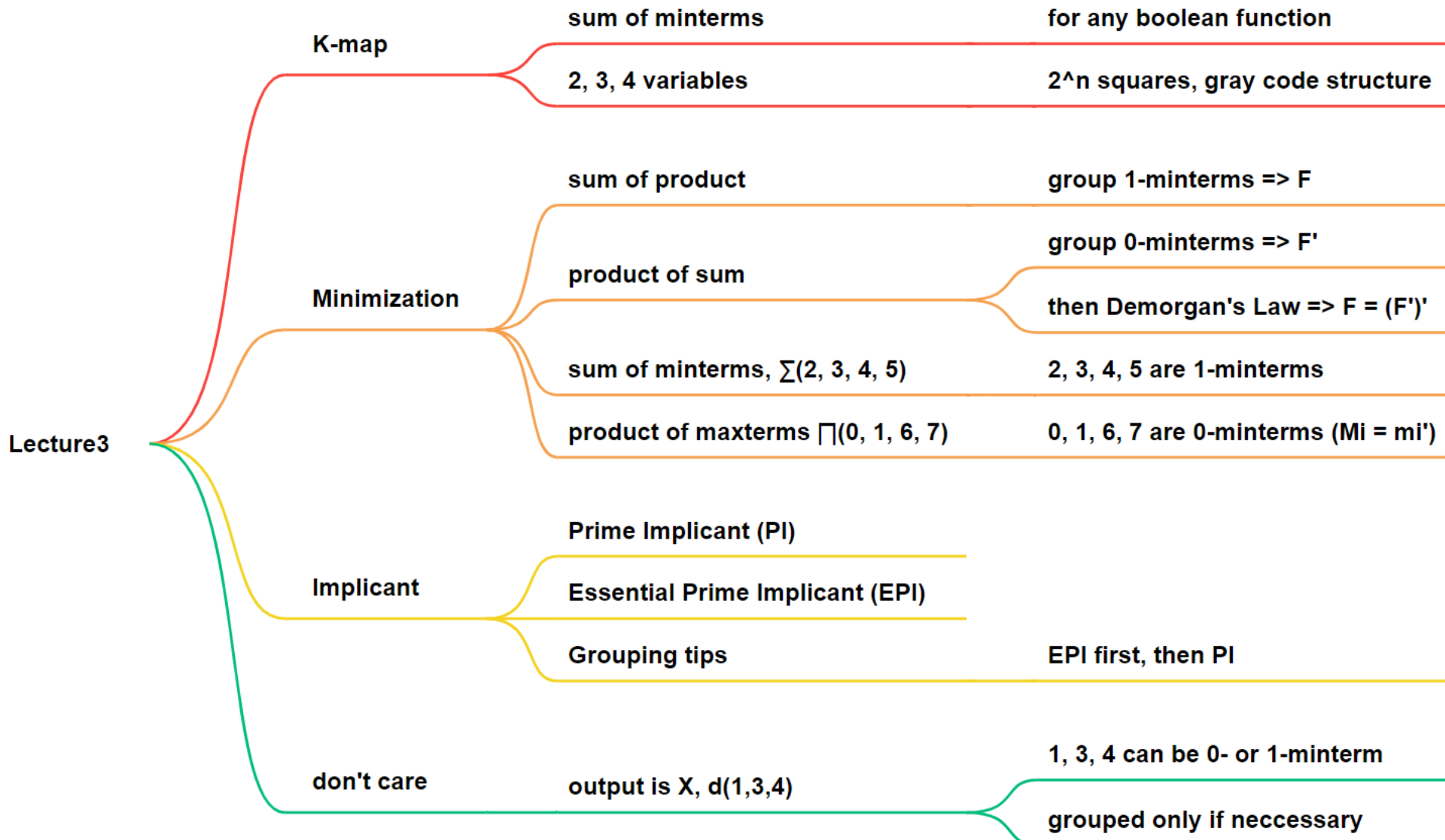

Recall: Logic Gates

AND



$$F = x \cdot y$$

x	y	F
0	0	0
0	1	0
1	0	0
1	1	1


OR



$$F = x + y$$

x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

Inverter

 

$$F = x'$$

x	F
0	1
1	0

Buffer



$$F = x$$

x	F
0	0
1	1

Recall: Logic Gates


NAND



$$F = (xy)'$$

x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

NOR

 

$$F = (x + y)'$$

x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

Exclusive-OR
(XOR)



$$F = xy' + x'y$$

$$= x \oplus y$$

x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

Exclusive-NOR
or
equivalence



$$F = xy + x'y'$$

$$= (x \oplus y)'$$





x	y	F
0	0	1
0	1	0
1	0	0
1	1	1

Outline


- **NAND Implementation**
- NOR Implementation
- Other Two-Level Implementations
- Exclusive-OR Function

Universal Gates


- NAND gates and NOR gates are called universal gates or universal building blocks.
 - Any type of gates or logic functions can be implemented by these gates.
 - NAND and NOR gates are easier to fabricate thus are frequently used.

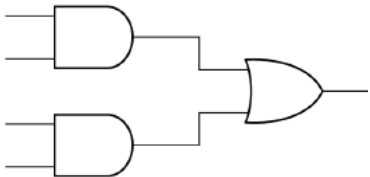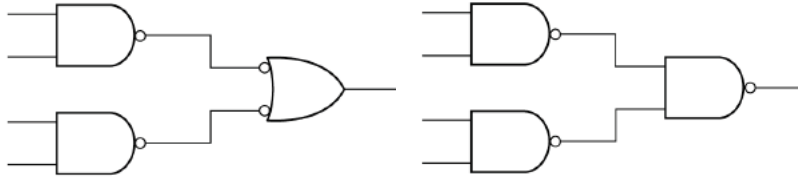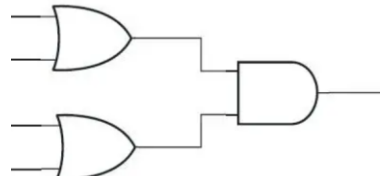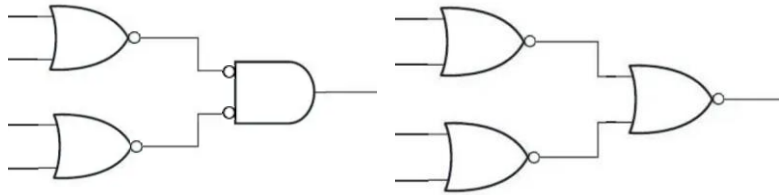	Standard form	Universal Gate implementation
Sum-of-products	<p>AND-OR</p> 	<p>NAND-NAND</p> 
Product-of-sums	<p>OR-AND</p> 	<p>NOR-NOR</p> 



NAND circuits

 



Inverter

 


AND

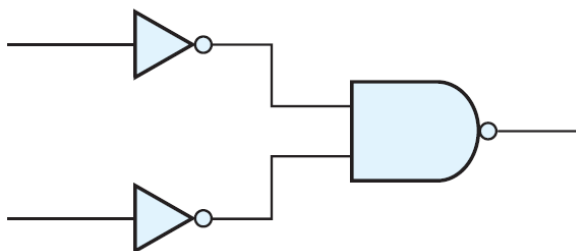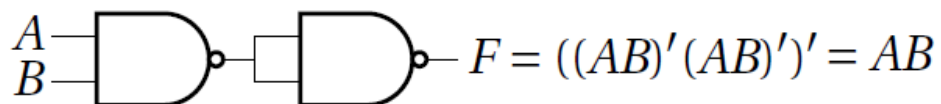

OR

 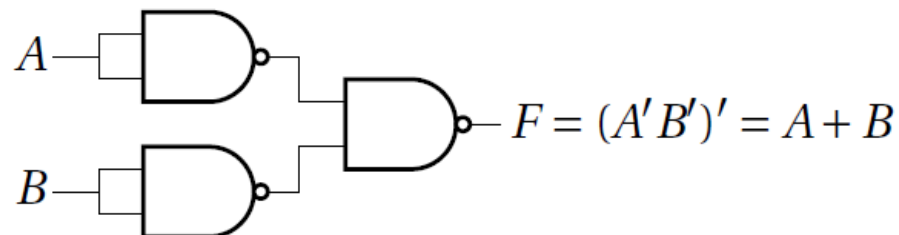

XOR

 


$$F = ((A(AB)')'((AB)'B)')'$$

$$= A(AB)' + (AB)'B = AB' + A'B = A \oplus B$$


hint: $AB' + A'B = AB' + A'B + AA' + BB'$

NAND circuits

 - To facilitate the conversion to NAND logic, it is convenient to define an alternative graphic symbol for the gate.
- AND-invert and Invert-OR are both NAND gates



(a) AND-invert

 

(b) Invert-OR




NAND-NAND Implementation

- A Boolean function can be implemented with two levels of NAND gates
 1. **Starting point** → Simplify the function in the form of **sum-of-products** (AND-OR circuit).
 2. Transfer it to 2-level NAND-NAND expression.
 - algebraically (**DeMorgan's Law**)
 - or graphically (**Bubble pushing**)
 3. Draw the corresponding NAND gate implementation. A 1-input NAND gate can be replaced by an inverter.

NAND-NAND Example1



- $F(A,B,C,D) = AB + CD$

   - Starting point: sum of products form \rightarrow done
- $F = AB + CD = ((AB + CD)')' = ((AB)' (CD)')' \rightarrow$ DeMorgan's
- Implementations: AND-OR / NAND-NAND (AND-Inv / Inv-OR)




NAND-NAND Example2

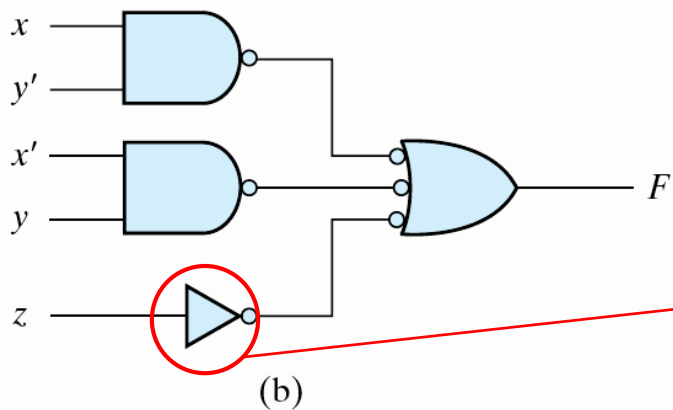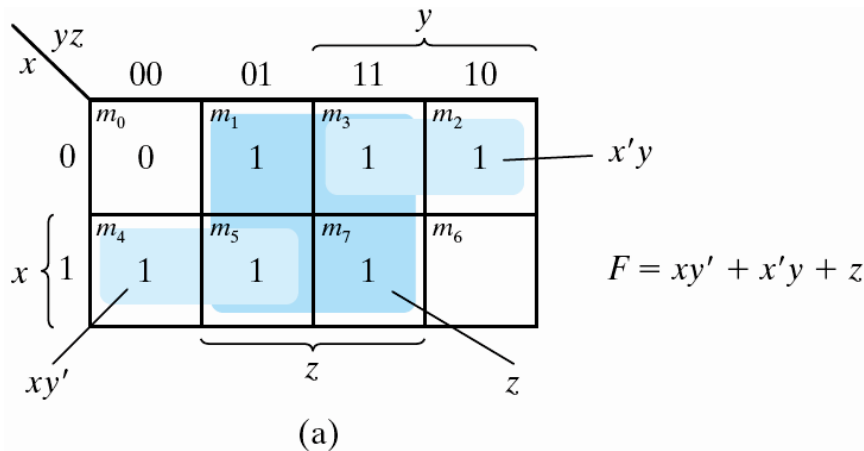- Example: Implement the following Boolean function with NAND gates
- $F(x,y,z) = \sum(1,2,3,4,5,7)$



or

 

NAND-NAND Example3

- Exercise: Implement the following Boolean function with NAND gates
- $F(A,B,C,D) = A'B'C'D + CD + AC'D$

NAND-NAND Example3

- $$F(A,B,C,D) = A'B'C'D + CD + AC'D$$


$$= A'B'C'D + (A+A')(B+B')CD + A(B+B')C'D$$

$$= A'B'C'D + ABCD + AB'CD + A'BCD + A'B'CD + ABC'D + AB'C'D$$


$$= \sum(1,3,7,9,11,13,15)$$
- $$F = CD + AD + A'D$$

$$= [(CD + AD + A'D)']' = [(CD)'(AD)'(A'D)']'$$

		C			
		CD			
		00	01	11	10
A	B	00	1	1	0
	01	0	0	1	0
	11	0	1	1	0
	10	0	1	1	0
		D			

 


or

 

Multilevel NAND Implementation

- Multilevel-NAND circuits conversion procedure
 - Convert all AND to NAND with AND-Invert graphic symbols
 - Convert all OR to NAND with Invert-OR graphic symbols
 - Check all the bubbles (inverter) in the diagram and insert possible inverter to keep the original function
- Example: $F(A,B,C,D) = A(CD+B)+BC'$
 - AND-OR logic \rightarrow NAND-NAND logic
 - For every bubble that is not compensated by another small circle along the same line, insert an inverter.

 AND \rightarrow AND + inverter
OR: inverter + OR = NAND




(a) AND-OR gates

Multilevel NAND Implementation

- Multilevel-NAND circuits conversion procedure
 - Convert all AND to NAND with AND-Invert graphic symbols
 - Convert all OR to NAND with Invert-OR graphic symbols
 - Check all the bubbles (inverter) in the diagram and insert possible inverter to keep the original function
- Example: $F(A,B,C,D) = A(CD+B)+BC'$
 - AND-OR logic \rightarrow NAND-NAND logic
 - For every bubble that is not compensated by another small circle along the same line, insert an inverter.

 
AND \rightarrow AND + inverter
OR: inverter + OR = NAND




(b) NAND gates

Multilevel NAND Implementation

 - Exercise: Implementing $F = (AB' + A'B)(C + D')$



(a) AND-OR gates

 



(b) NAND gates

Outline

- NAND Implementation
- **NOR Implementation**
- Other Two-Level Implementations
- Exclusive-OR Function


NOR-NOR Implementation

  - NOR-NOR is the dual of the NAND-NAND implementation
 - All procedures and rules for NOR logic are the duals of the corresponding which developed for NAND logic.




NOR-NOR Implementation

 - To facilitate the conversion to NOR logic, it is convenient to define an alternative graphic symbol for the gate.



(a) OR-invert

 

(b) Invert-AND



NOR-NOR Implementation

- Procedure of NOR-NOR implementation
 - **Starting point** → Simplify the function in the form of **product-of-sum** (OR-AND circuit).
 - Transfer it to 2-level NOR-NOR expression.
 - algebraically (**DeMorgan's Law**)
 - or, graphically (**Bubble pushing**)
 - Draw the corresponding NOR gate implementation. A 1-input NOR gate can be replaced by an inverter.

sum-of-product (AND-OR) \Rightarrow NAND-NAND
product-of-sum (OR-AND) \Rightarrow NOR-NOR

NOR-NOR Example1

  - Example: Implement the following Boolean function with NAND gates
- $F = (A + B)(C + D)E$
 - Starting point: product of sums form \rightarrow done
 - $F = (A+B)(C+D)E = ((A+B)(C+D)E)''$
 - $= ((A+B)' + (C+D)' + E')' \rightarrow$ DeMorgan's
 - Implementations:



NOR-NOR Example2

- Example



$$F(x,y,z) = \sum(1,2,3,4,5,7)$$

		y			
		yz		11	10
x	0	m_0 0	m_1 1	m_3 1	m_2 1
	1	m_4 1	m_5 1	m_7 1	m_6 0

$$F' = x'y'z' + xyz'$$

$$F = (F')' = (x'y'z' + xyz')'$$

$$= ((x+y+z)' + (x'+y'+z))'$$

  


Multilevel NOR Implementation


- Change the OR gates to NOR gates with OR-invert graphic symbols and the AND gate to a NOR gate with an invert-AND graphic symbol.

- Example:

- $F = (AB' + A'B)(C + D')$

 

- $F = (AB + E)(C + D)$

 


Quiz



1. Simplify the Boolean function $F(x,y,z) = x'y + yz + x'y'z'$ into sum of product form, using map method.
2. Simplify the previous function into product of sum form.
3. True/False: any logic circuit can be implemented with NOR gates
4. Which of the following Boolean function is correct for the logic diagram?

- a) 1
- b) 0
- c) B'
- d) A

 

5. Simplify the following Boolean function F, together with the don't-care conditions d. $F(A,B,C,D) = \sum(0,6,8,12,14)$, $d(A,B,C,D) = \sum(2,4,10)$

Outline

- NAND Implementation
- NOR Implementation
- **Other Two-Level Implementations**
- Exclusive-OR Function

Two-Level Forms

- AND/NAND/OR/NOR have 16 possible combinations of two-level forms
- Eight of them **degenerate** to a single operation
 - AND-AND \Rightarrow AND
 - OR-OR \Rightarrow OR
 - AND-NAND \Rightarrow NAND
 - OR-NOR \Rightarrow NOR
 - NAND-NOR \Rightarrow AND
 - NOR-NAND \Rightarrow OR
 - NAND-OR \Rightarrow NAND
 - NOR-AND \Rightarrow NOR


Two-Level Forms

- Eight are **non-degenerate** forms
- AND-OR \Rightarrow standard sum-of-products
- NAND-NAND \Rightarrow standard sum-of-products
- OR-AND \Rightarrow standard product-of-sums
- NOR-NOR \Rightarrow standard product-of-sums
- NAND-AND/AND-NOR \Rightarrow AND-OR-INVERT (AOI)
 - **complement** of sum-of-products
- OR-NAND/NOR-OR \Rightarrow OR-AND-INVERT (OAI)
 - **complement** of product-of-sums


AND-OR-Invert Implementation

- NAND-AND = AND-NOR = AOI

 
- $F(A,B,C,D,E) = (AB + CD + E)'$
- $F'(A,B,C,D,E) = AB + CD + E$ (sum of products)
- An AND-OR implementation requires an expression in sum-of-products form.
- The AND-OR-INVERT implementation is similar, except for the inversion.



(a) AND-NOR

 

(b) AND-NOR

 


(c) NAND-AND


Combine 0's in K-map to simplify F' in product-of-sums and then invert the results

OR-AND-Invert Implementation

 
- OR-NAND = NOR-OR = OAI
 - $F(A,B,C,D,E) = ((A+B)(C+D)E)'$
 - $F' = (A+B)(C+D)E$ (product of sums)
 - The AND-OR-INVERT implementation requires an expression in product-of-sums form.



(a) OR-NAND

 

(b) OR-NAND

 

(c) NOR-OR

Combine 1's in K-map to simplify F' in product-of-sums and then invert the results

AOI & OAI Example

- Example

		y			
		yz	00	01	11
x	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

$x'y'z'$ points to m_0
 xyz points to m_6
 x is grouped by a bracket on the left
 z is grouped by a bracket at the bottom

$$F = x'y'z' + xyz'$$

$$F' = x'y + xy' + z$$

- AND-OR

- $F = x'y'z' + xyz'$

- NAND-NAND

- $F = ((x'y'z')'(xyz'))'$

- OR-AND

- $F' = x'y + xy' + z \rightarrow F = z'(x' + y)(x + y')$

- NOR-NOR

- $F' = x'y + xy' + z \rightarrow F = (z + (x' + y)' + (x + y')')'$

- AOI

- $F' = x'y + xy' + z \rightarrow F = (x'y + xy' + z)'$

- OAI

- $F = x'y'z' + xyz' \rightarrow F' = (x + y + z)(x' + y' + z) \rightarrow F = ((x + y + z)(x' + y' + z))'$


Exclusive-OR Function

- Exclusive-OR (XOR)
 - $x \oplus y = xy' + x'y$
- Exclusive-NOR (XNOR or equivalency)
 - $(x \oplus y)' = xy + x'y'$
- Some identities
 - $x \oplus 0 = x$
 - $x \oplus 1 = x'$
 - $x \oplus x = 0$
 - $x \oplus x' = 1$
 - $x \oplus y' = x' \oplus y = (x \oplus y)'$
- Commutative and associative
 - $A \oplus B = B \oplus A$
 - $(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$


Exclusive-OR Implementations

- Implementations

 - $(x' + y')x + (x' + y')y = xy' + x'y = x \oplus y$



(a) With AND-OR-NOT gates

 


(b) With NAND gates

Outline


- NAND Implementation
- NOR Implementation
- Other Two-Level Implementations
- **Exclusive-OR Function**

Odd function

- The XOR operation with three or more variables can be converted into an ordinary Boolean function by replacing the \oplus with its equivalent Boolean expression.
- $A \oplus B \oplus C = (AB' + A'B)C' + (AB + A'B')C$
 $= AB'C' + A'BC' + ABC + A'B'C$
 $= \sum(1, 2, 4, 7)$
- Odd function (XOR) \rightarrow if **odd** number of variables are equal to 1, then $F = 1$.
- Even function (XNOR) \rightarrow if **even** number of variables are equal to 1, then $F = 1$.

 

(a) 3-input odd function

 

(b) 3-input even function

Recall: Error-Detecting Code

- Error-Detecting Code

- An eighth bit is sometimes added to the ASCII character to indicate its parity.
- A **parity bit** (校验位) is an extra bit included with a message to make the total number of 1's either even or odd.

- Example:

ASCII A = 1000001

With even parity

01000001


With odd parity

11000001

Even-Parity-Generator Truth Table

Three-Bit Message			Parity Bit
x	y	z	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 
XOR functions can be used for parity generator and parity checker




Parity Generation and Checking

- $P = xy'z' + x'yz' + xyz + x'y'z$
 $= \sum(1, 2, 4, 7) - \text{odd function}$

x	y	z	Parity bit p
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

even parity generator

 

even parity checker

- Parity Generation and Checking
 - A even parity bit: $P = x \oplus y \oplus z$
 - Even Parity check: $C = x \oplus y \oplus z \oplus P$
 - $C=1$: one bit error or an odd number of data bit error
 - $C=0$: correct or an even # of data bit error